

SOLUTION FOR THE EXPERIMENTAL COMPETITION

Coal tablet (15.0 points)

Part 1. Ohm's law (7.0 points)

To check whether Ohm's is in power in this case the circuit shown on the right should be connected such that the multimeter in voltmeter mode is used to measure the voltage across the tablet R_C and the resistor $R_0 = 1,0 \text{ Ohm}$. The latter is equal to the electric current.

The results for two given weights are presented in table 1.


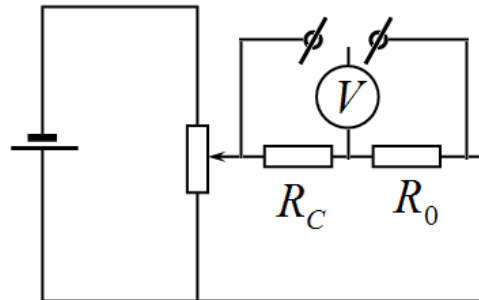


Table 1

$m = 200 \text{ g}$		$m = 400 \text{ g}$	
U, V	I, mA	U, V	I, mA
6,43	120,0	6,09	142,0
4,69	89,0	4,37	96,0
4,08	72,7	3,36	68,0
3,27	56,6	2,7	54,5
2,41	37,0	2,02	39,2

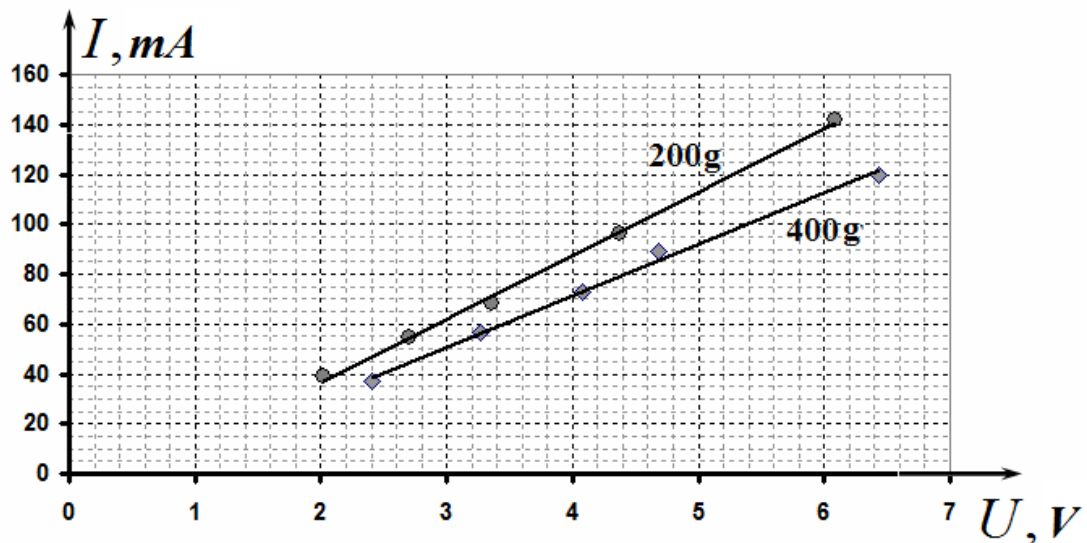The graphs of the obtained dependences are shown below.



With a high degree of accuracy these dependences are linear which means that the resistance is independent of the voltage and Ohm's law holds.

To calculate the resistances it is required to use the least square method. The result are summarized as follows

$$200 \text{ g} - a = (21 \pm 2) \frac{\text{mA}}{\text{V}} \quad b = (-10 \pm 11) \text{mA};$$

$$400 \text{ g} - a = (25 \pm 2) \frac{\text{mA}}{\text{V}} \quad b = (-10 \pm 8) \text{mA}$$

Consequently, the corresponding resistances are found as


$$R_{200} = \frac{1}{a} = (47 \pm 5) \text{ Ohm} \quad R_{400} = \frac{1}{a} = (40 \pm 3) \text{ Ohm}$$

Part 2. Mechanical stress and resistance (5.0 points)


The resistance can be directly measured by the multimeter. And the results are shown in table 2.

Table 2.

m, g	R, Ohm	R^{-1}, Ohm^{-1}
100	76	0,0132
200	56	0,0179
300	44	0,0227
400	36	0,0278
500	32	0,0313
600	30	0,0333

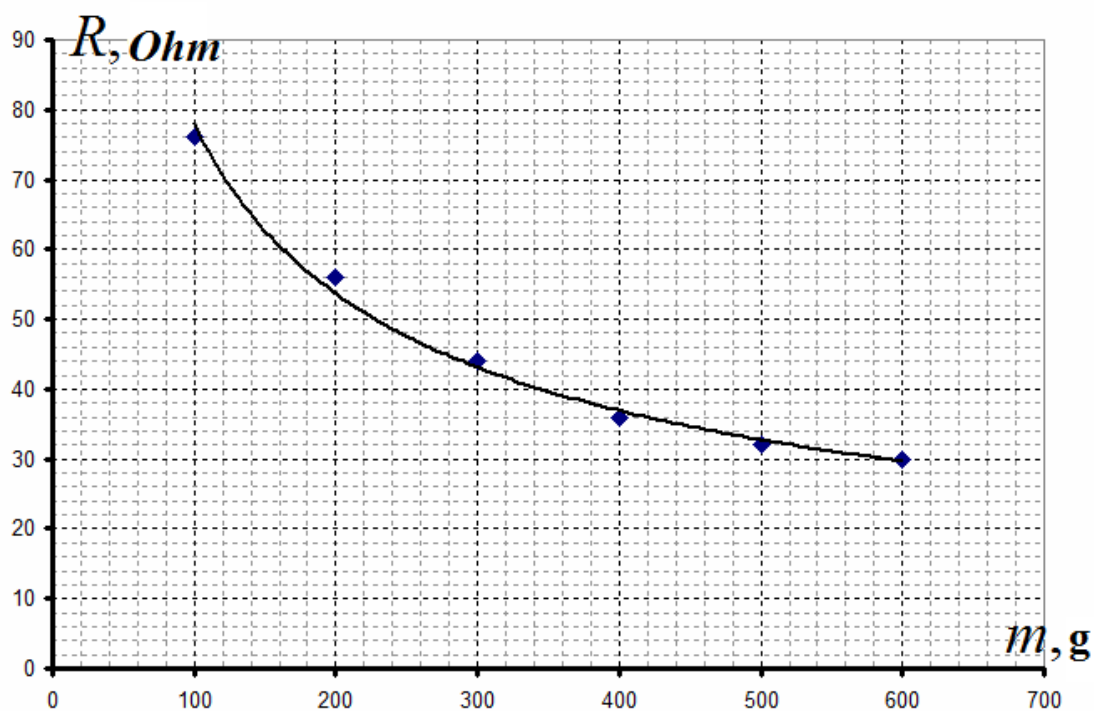

It is seen from the graph above that the dependence is actually inversely proportional. Thus, the conductivity is approximately proportional to the mass of weights.

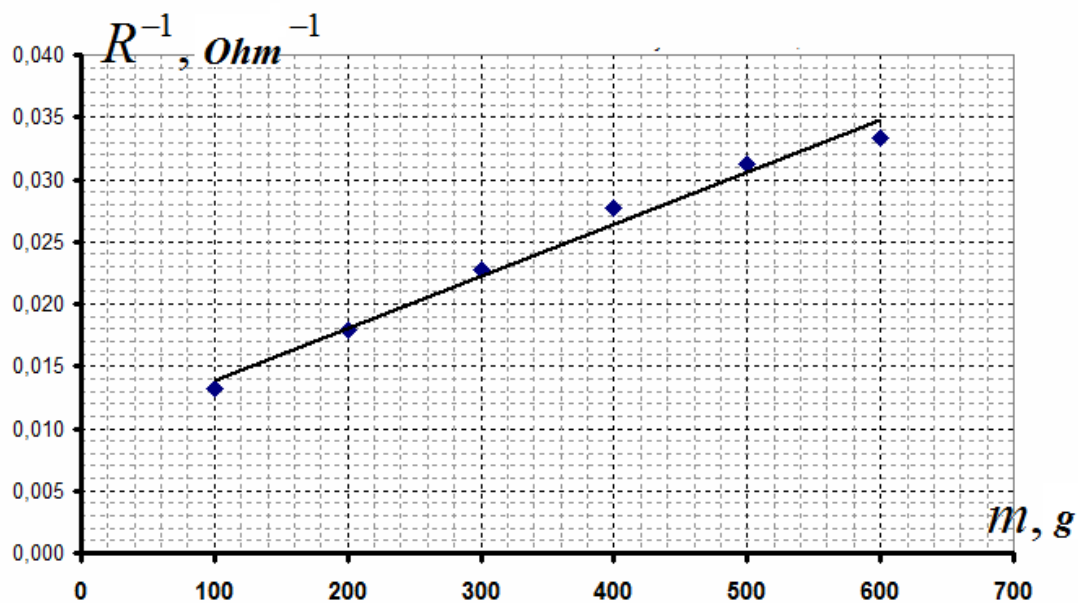


Part 3. Designing scales (3.0 points)

The obtained results demonstrate that the current in the circuit shown above is proportional to the mechanical stress on the tablet. That is why the circuit for electronic scales should be the same and the voltage must be measured across the resistor R_0 . The “readings” of the scales as a function of the mechanical stress are presented in table 3 and in the corresponding graph.

Table 3.

m, g	U, mV
100	140
200	155
300	168
400	180
500	195
600	210

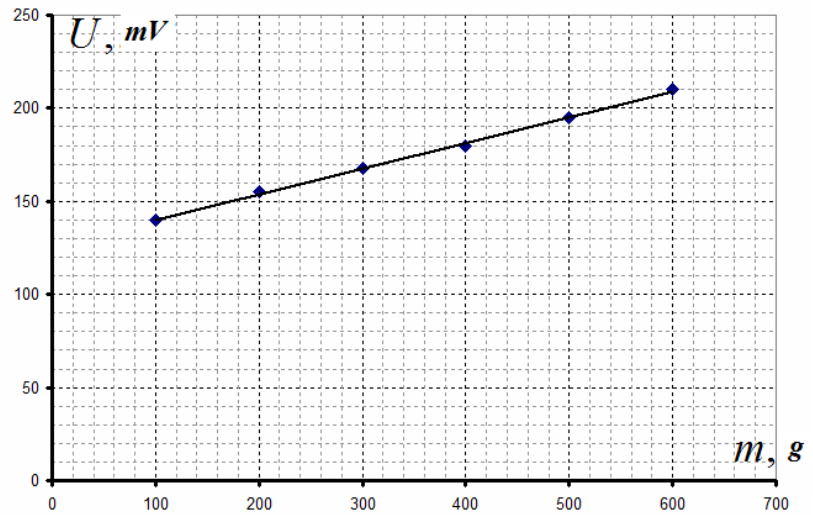

Grading scheme

	Content	Points	Total
3.1	The electrical circuit allows one to measure the electric current and the voltage.	1,0	1.0
	Setting up the mechanical stress according to lever rule	0,5	0,5
	Taking measurements: - no less than 5 points for each dependence (3-4. less than 3); - the voltage up to 6 V (up to 4 V, or less); Linear dependences are obtained	2x1,0 (2x0,5, 0) 2x0.5 (2x0,25,0) 2x0,25	3,5
	Plotting the graph: Axis are labeled and ticked, All points are present in the graph; Smooth lines are drawn	0,1 0,2 0,2	0,5
	Calculation of the resistances: (acceptable range – 30-60 Ohm) - using LSM; - graphically; - by two points Errors are evaluated	2x0,5 (2x0,4) (2x0,25) 2x0,25	1,5
2.1	Taking measurements: (the acceptable range 100-30 Ohm) - no less than 6 points; - the resistance decreases/increases at least twice; - repeated measurements are taken; - the obtained dependence is inversely proportional;	1,5 1,0 0,5 0,5	3,5
2.2	Plotting the graph Axis are labeled and ticked, All points are present in the graph; Smooth lines are drawn	0,1 0,2 0,2	0,5
2.3	Linearization is made	0,5	0,5
	The graph of the linearized dependence	0,5	0,5
3.1	The circuit is to measure the current	1,5	1,5
	Plotting the calibrating graph: no less than 5 points; Axis are labeled and ticked, All points are present in the graph;	0,5 0,5	1,5
	Smooth lines are drawn	0,5	
	Total	15	